

Passive Filters

Filter Applications

- Filters are specifically used to
 - remove unwanted frequency components from the signal
 - to enhance wanted ones
 - or both.
- Filters are essential building blocks in many systems,
 - Example: used in communication and instrumentation systems
- A common need for filter circuits is in high-performance stereo systems, where certain ranges of audio frequencies need to be amplified or suppressed for best sound quality and power efficiency

Filter Characteristics

- Filter is an electrical network that modifies the amplitude and phase characteristics of a signal with respect to frequency
- In electronic systems, filters are useful in emphasizing signals in certain frequency ranges and reject signals in other frequency ranges.

Different types of Filters

- **Low-pass filter:** low frequencies are passed; high frequencies are attenuated.
- **High-pass filter:** high frequencies are passed; low frequencies are attenuated.
- **Band-pass filter:** only frequencies in a frequency band are passed.
- **Band-stop filter or band-reject filter:** only frequencies in a frequency band are attenuated

- Filter is characterized by two important observations
 - **Transfer Function or Transfer Characteristics:** A mathematical function describing the output response of a filter system to the input or stimulus. Transfer function in filters is studied as a frequency response
 - **Phase response:** How the phase of filter changes with frequency
- The order of the filter is decided by the order of the differential equation that need to be solved.
 - 1st order differential equation- 1st order filter
 - 2nd order differential equation- 2nd order filter
 - Important properties of filter
- **3 dB Frequency or cut-off frequency:** The frequency at which the transfer function becomes half.



RC Low Pass Filters

- Low pass filter passes low frequency signals and attenuates high frequency signals.
- Consider an input signal v_{in} . Output v_{out} is taken across capacitor.
- Transfer function $H(\omega)$:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_C}{V_R + V_C}$$

$$H(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

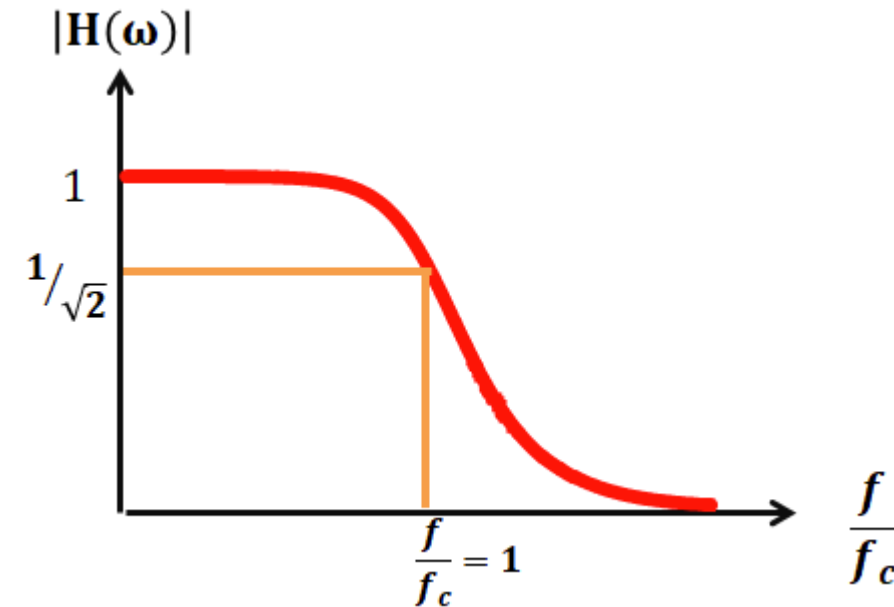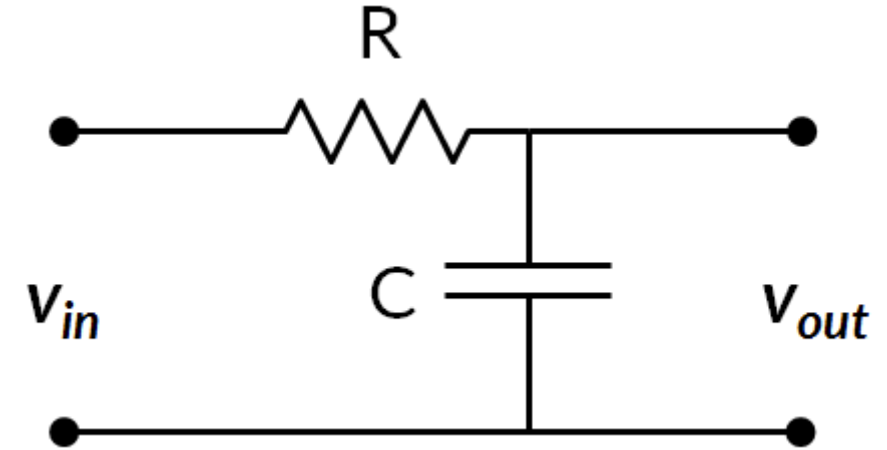

RC Low Pass Filters

Cut-off Frequency (f_c)

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$


$$f_c = \frac{1}{2\pi RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

Phase Angle (ϕ)

$$\phi = -\tan^{-1}(\omega RC)$$
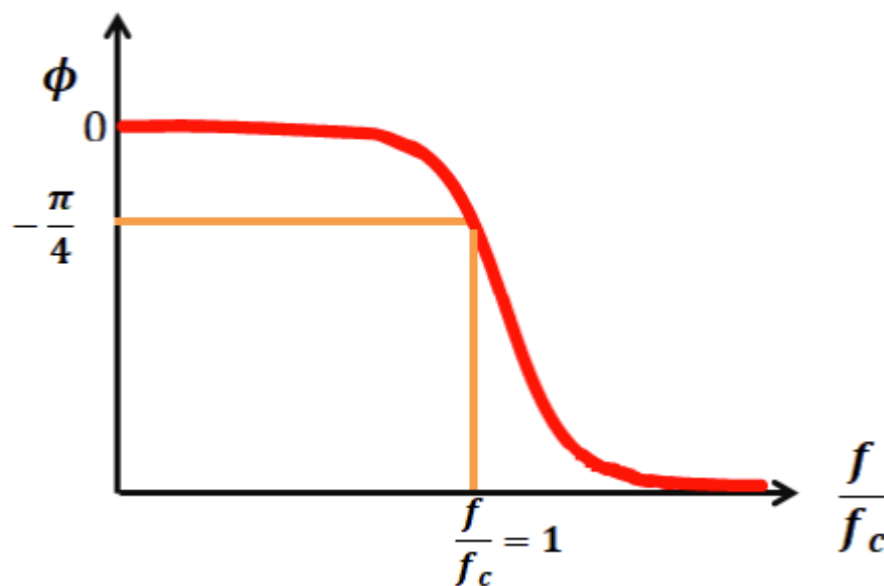
$$\phi = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right) = -\tan^{-1}\left(\frac{f}{f_c}\right)$$





RC High Pass Filters

- High pass filter passes high frequency signals and attenuates low frequency signals
- Consider an input signal v_{in} . Output v_{out} is taken across resistor.
- Transfer function $H(\omega)$:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_R}{V_R + V_C}$$

$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

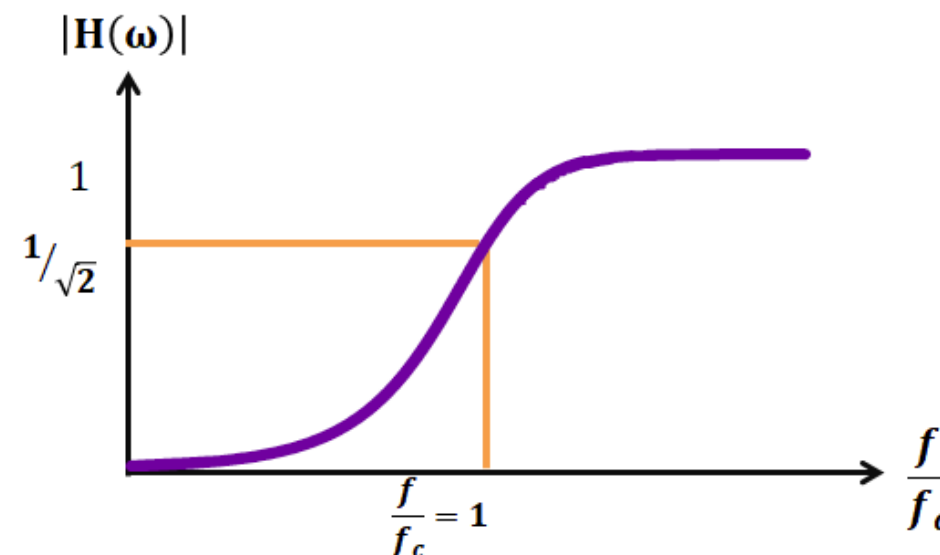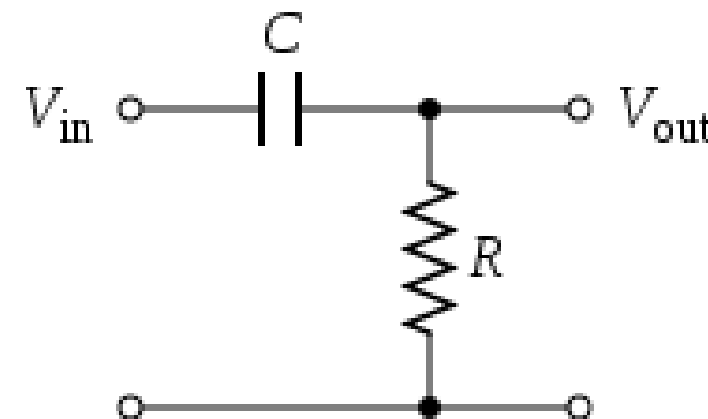

RC High Pass Filters

Cut-off Frequency (f_c)

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$\frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$


$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$

Phase Angle (ϕ)

$$\phi = \frac{\pi}{2} - \tan^{-1}(\omega RC)$$

$$= \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$
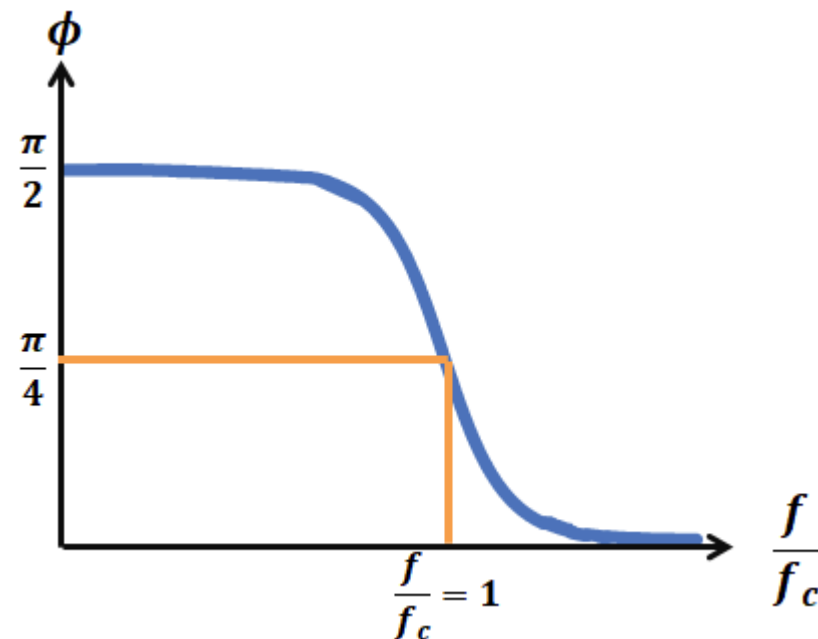
$$= \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_c}\right)$$





RL Low Pass Filters

- Transfer function $H(\omega)$:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_R}{V_R + V_L}$$

$$H(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}$$

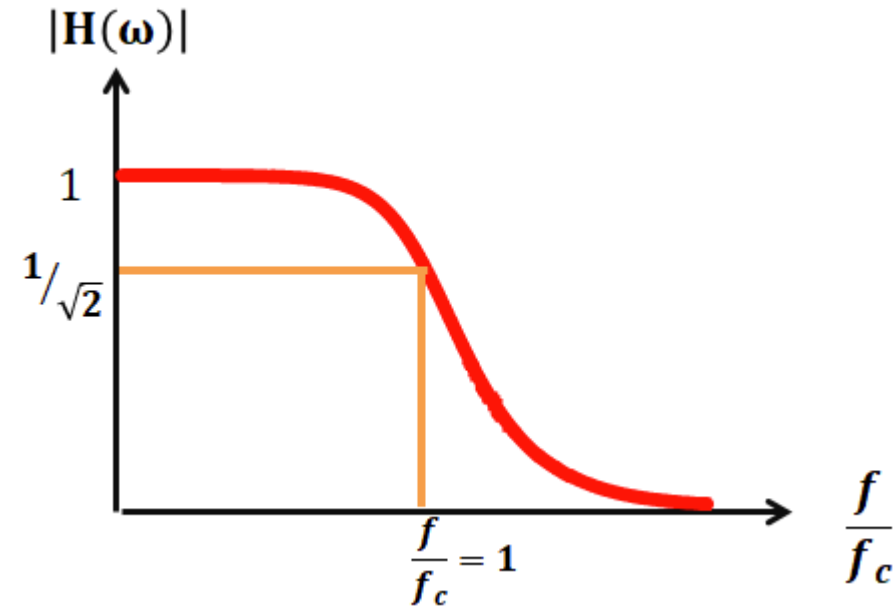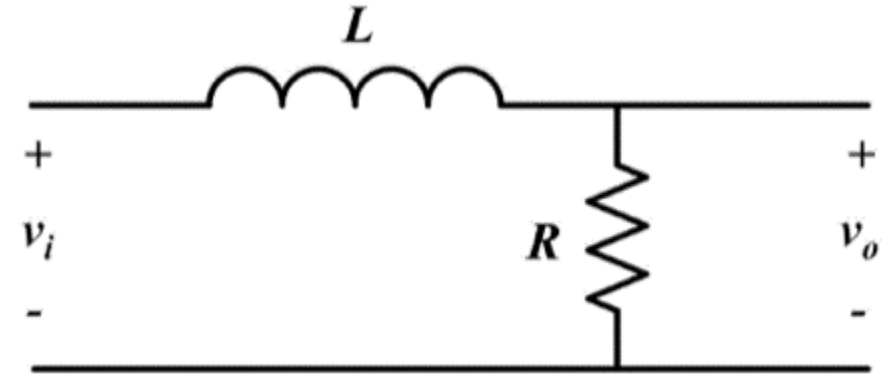

RL Low Pass Filters

Cut-off Frequency (f_c)

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} = \frac{1}{\sqrt{2}}$$


$$\omega_c = \frac{R}{L}$$

$$f_c = \frac{R}{2\pi L}$$

Phase Angle (ϕ)

$$\phi = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$
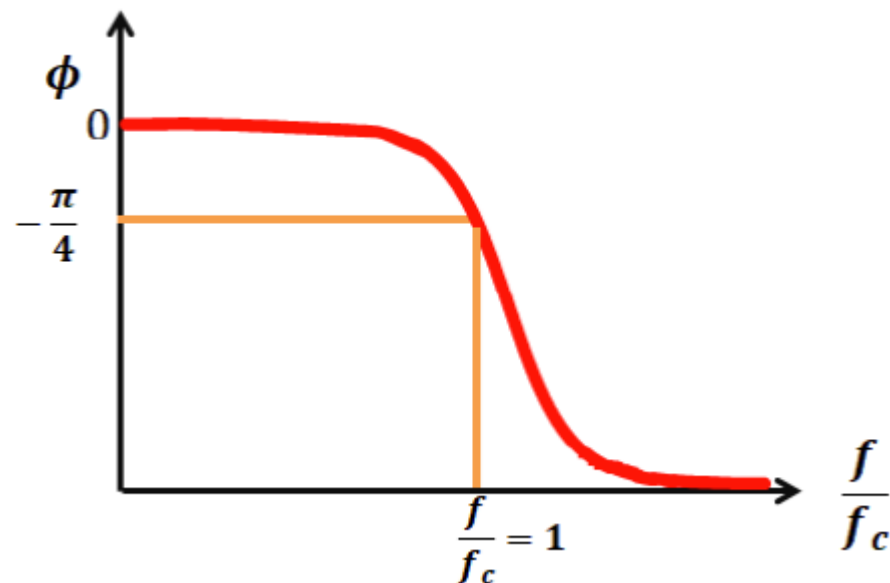
$$\phi = -\tan^{-1} \left(\frac{\omega}{\omega_c} \right) = -\tan^{-1} \left(\frac{f}{f_c} \right)$$





RL High Pass Filters

- Transfer function $H(\omega)$:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_L}{V_R + V_L}$$

$$H(\omega) = \frac{j\omega L}{R + j\omega L} \qquad H(\omega) = \frac{1}{1 + \frac{R}{j\omega L}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}}$$

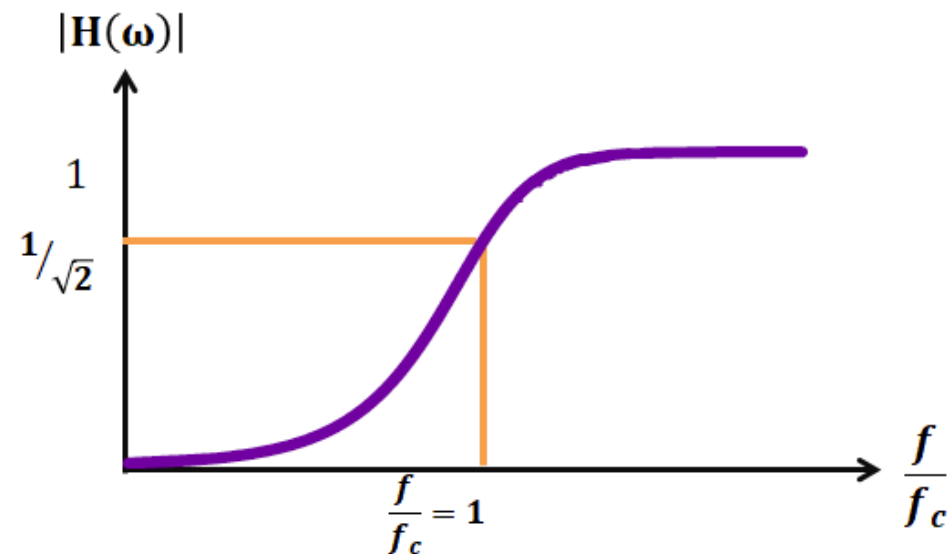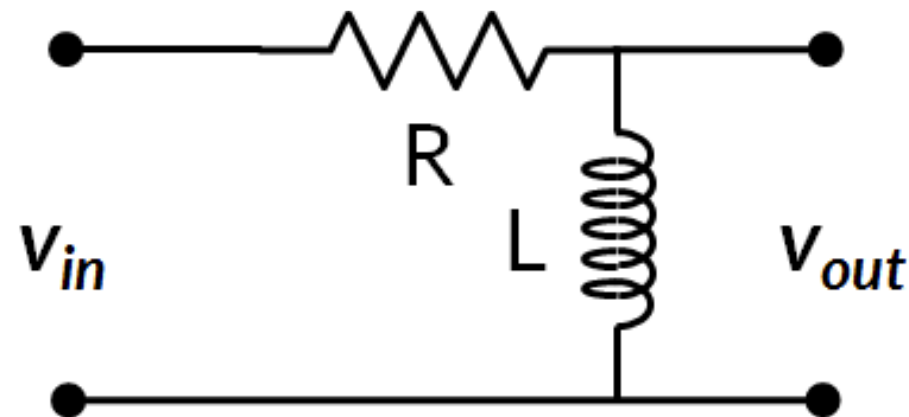

RL High Pass Filters

Cut-off Frequency (f_c)

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{R}{L}$$

$$f_c = \frac{R}{2\pi L}$$

Phase Angle (ϕ)

$$\phi = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\phi = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$$= \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_c}\right)$$

