



Department of ECE, Bennett University



EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-15

Topics Covered: Number System and Digital Logic

- Convert the following number in to binary:
 i) 125 ii) 89 iii) 24 iv) 56 v) 12.9 vi) 9.286 vii) 17.987 viii) 0.987
 ix) 0.575 x) 0.485 xi) 0.355 xii) 0.245 xiii) 0.075
- Represent the numbers as used in a computer using sign bit representation, 1's complement and 2's complement.
 i) -12 ii) -38 iii) -189 iv) -267
- Simplify the following by converting the numbers in to binary:
 i) $128 + 29$ ii) $287 - 128$ iii) $217 - 317$ iv) $77 - 84$ v) $92 - 13$
- Draw the logic circuit represented by the following expressions:
 i) $\bar{A}B + A\bar{B}$ ii) $AB + \bar{A}\bar{B} + \bar{A}BC$ iii) $\bar{A}B(C + \bar{D})$
- Using Boolean algebra, simplify the following expressions as much as possible and draw the resultant logic function using universal gates.
 i) $A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C$ ii) $A(A + \bar{A}B)$ iii) $\bar{A}\bar{B}C + \overline{(A + B + \bar{C})} + \bar{A}\bar{B}\bar{C}D$
 iv) $(B + BC)(B + \bar{B}C)(B + D)$
- Convert the following expressions to standard SOP form.
 i) $(A + B)(C + \bar{B})$ ii) $(C\bar{B} + A)C$
- Convert the following expressions to standard POS form.
 i) $AB + CD(\bar{A}\bar{B} + CD)$ ii) $AB(\bar{B}\bar{C} + BD)$
- Determine which of the following logic circuits are equivalent.

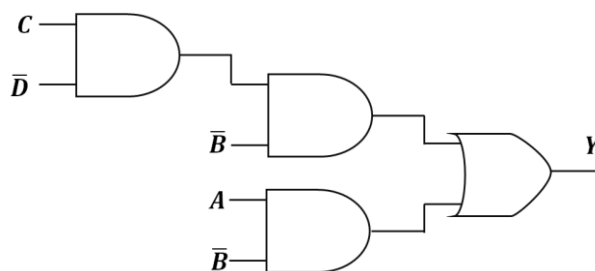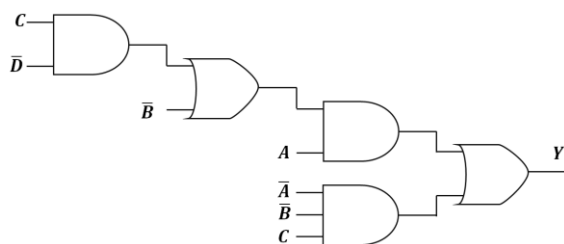

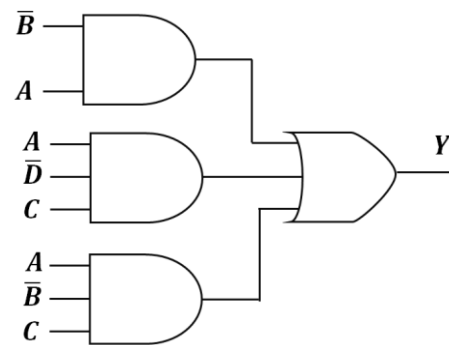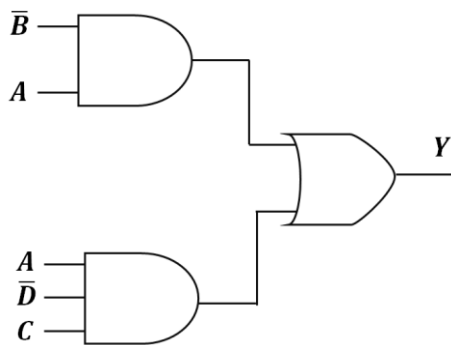

9. For the truth tables given below, derive a standard SOP and POS form.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

----- END OF QUESTIONS -----

Think:

How to represent negative fractions in binary (2's complement form)?