

# Discharging a Capacitor

- Coulombic repulsion between charges already existing the plates creates a force that lets charges to discharge out of the capacitor once the voltage on the charge in the capacitor is decreased
- Coulombic repulsion decreases as more charges are removed from the capacitor plates.
- Initially, voltage across the capacitor decreases rapidly as charge is removed from the plates.
- As more and more charge is removed, voltage across the capacitor decreases more slowly as it becomes difficult to force the remaining charge out of the capacitor.

# Discharging a Capacitor

- Applying KVL

$$V_R + V_C = 0$$

$$iR + \frac{q}{C} = 0 \quad \frac{dq}{dt}R + \frac{q}{C} = 0$$

$$\int \frac{dq}{q} = - \int \frac{dt}{RC} \quad \ln q = -\frac{t}{RC} + C_1$$


$$q = e^{-\frac{t}{RC}} + C_1 \quad q = C_2 e^{-\frac{t}{RC}}$$

Substitute boundary condition: at  $t = 0$ , Voltage across  $C = V$ ,  $q = VC$

$$C_2 = VC \quad q = VC e^{-\frac{t}{RC}}$$


$$V_C = \frac{q}{C} = V e^{-\frac{t}{RC}}$$
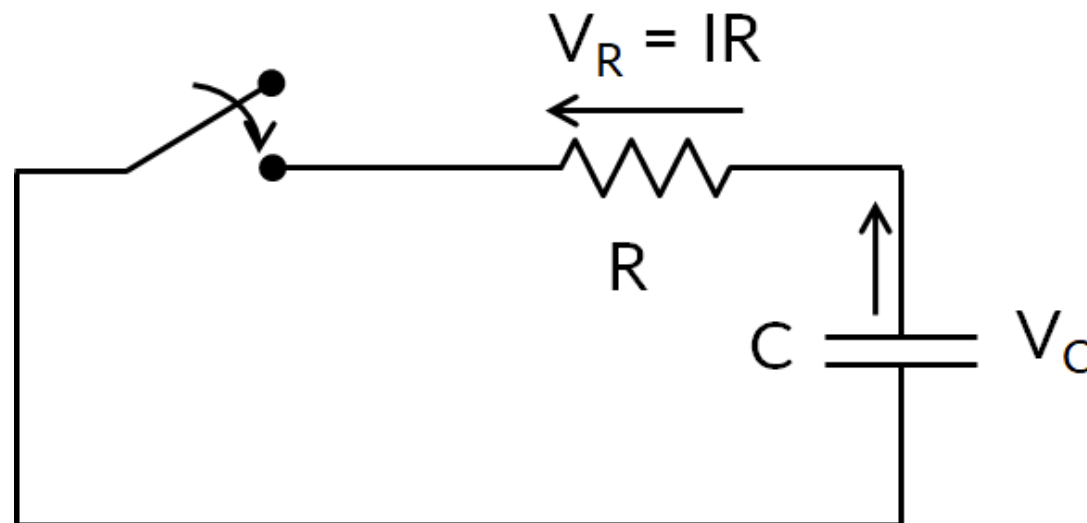
$$i = \frac{dq}{dt} = -\frac{V}{R} e^{-\frac{t}{RC}}$$



- Note that the negative sign indicate that the current is opposite to the charging current's direction

## Discharging a Capacitor


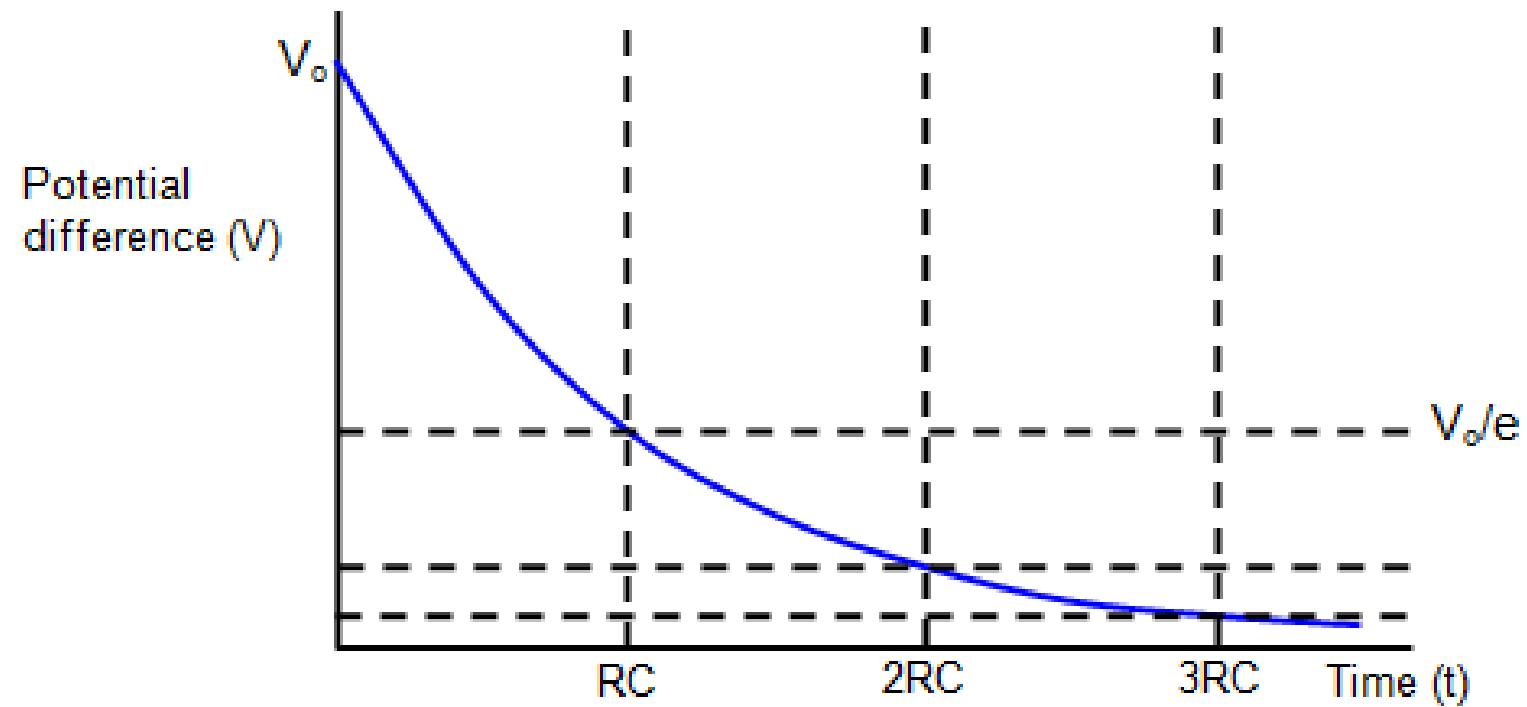


# Inductors


- Inductor stores energy in a magnetic field created by an electric current flowing through it.
- Inductor opposes change (chokes) in current flowing through a conductor.
- Current through an inductor is continuous; voltage can be discontinuous.
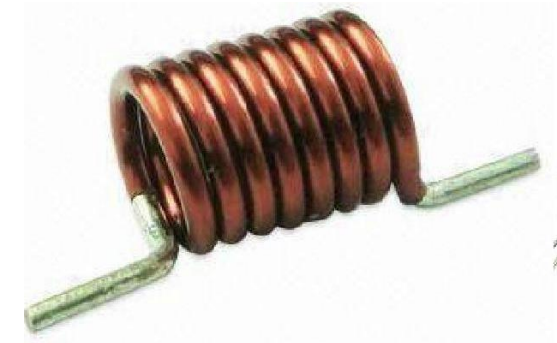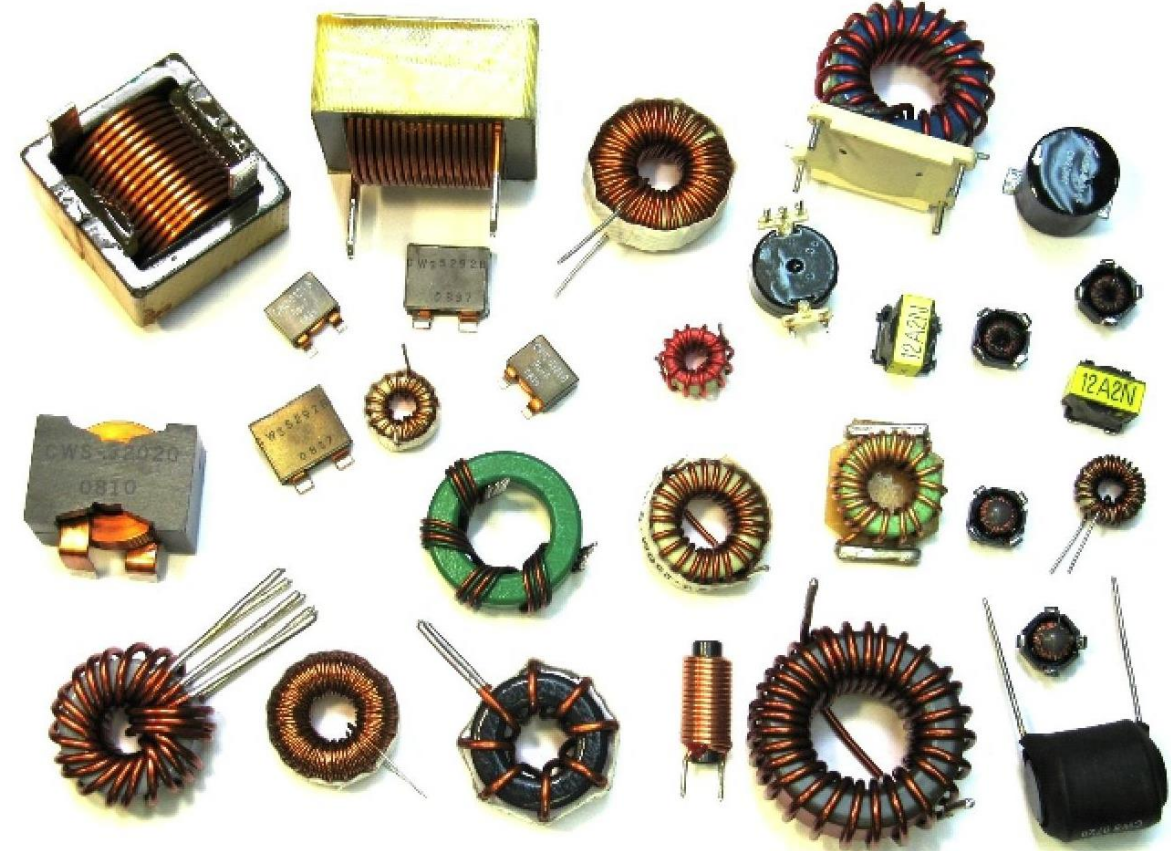
## Structure

- Generally formed by a coil of conducting wire
- Conducting wire is usually wrapped around a solid core.
- In the absence of a core, the inductor is said to have an 'air core'.



## Inductor symbols

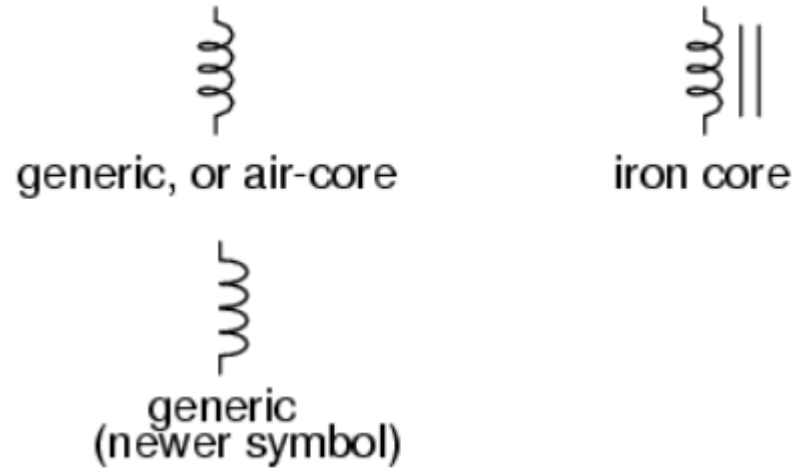

## Calculations of L

$$L = \frac{N^2 \mu A}{l} = \frac{N^2 \mu_0 \mu_r A}{l}$$


$N$  is the number of turns of wire

$A$  is the cross-sectional area of the toroid in  $\text{m}^2$ .

$\mu_r$  is the relative permeability of the core material


$\mu_0$  is the vacuum permeability ( $4\pi \times 10^{-7} \text{ H/m}$ )

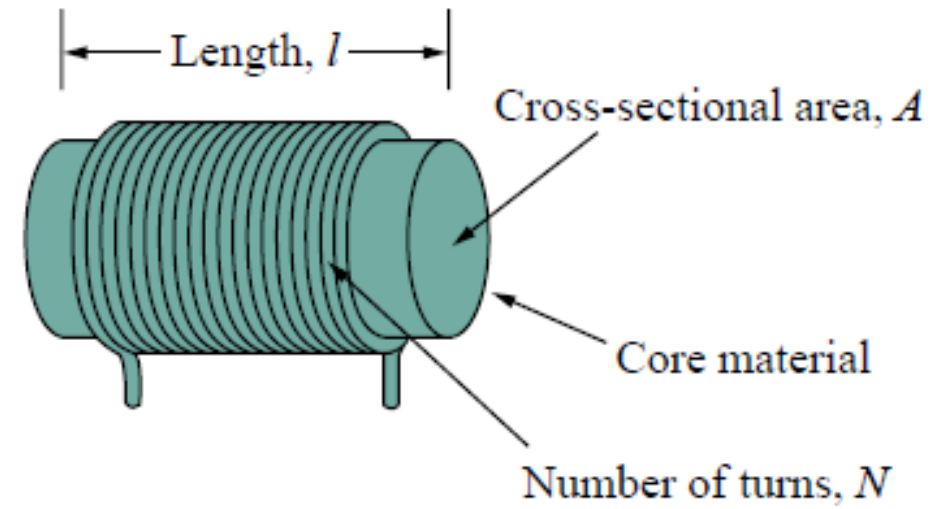$l$  is the length of the wire used to wrap the toroid in meters


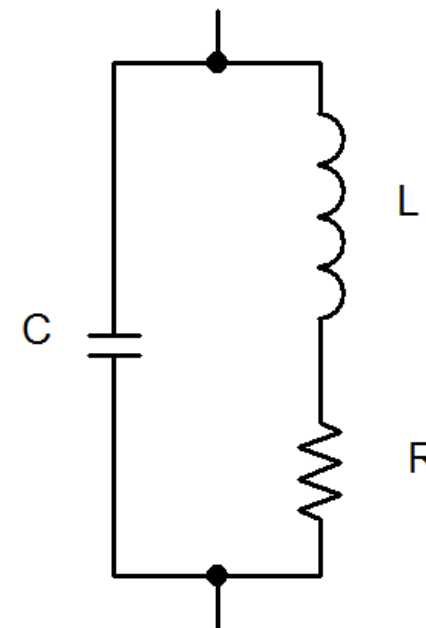
## Properties of an Inductor

- Inductor acts like a short circuit in steady state.
- Current through an inductor must be continuous, meaning there are no abrupt changes to the current but there can be abrupt changes in the voltage across an inductor.
- No energy or power is dissipated by an ideal inductor. Ideal inductor absorbs energy or power from the circuit when storing energy and restores energy into circuit while discharging




## Properties of a Real Inductor

- Due to resistive losses and capacitive coupling between turns of wire
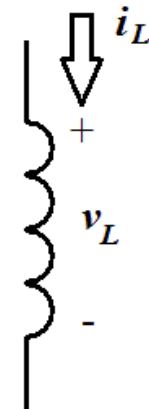
## Sign Convention

- When current flows into the positive side of the voltage across the inductor, the current is positive, and the inductor is dissipating power
- When an inductor releases energy back into the circuit, the sign of the current is negative.



## Current Voltage Relationship

- the voltage across the inductor is directly proportional to the time rate of change of the current.

$$v_L = L \frac{di}{dt}$$

$$i_L = \frac{1}{L} \int_{t_0}^{t_1} v_L dt$$

# Current Voltage Relationship

Let  $I_L = I_0 \sin(\omega t)$

$$v_L = L \frac{d}{dt} (I_0 \sin(\omega t))$$

$$v_L = \omega L I_0 \cos(\omega t)$$

$$= \omega L I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

- Voltage across inductor leads current through inductor

by  $\frac{\pi}{2}$

Let  $I_L = I_0 e^{j\omega t}$   $v_L = L \frac{di}{dt}$

$$v_L = L \frac{d}{dt} (I_0 e^{j\omega t}) = j\omega L I_0 e^{j\omega t}$$

$$v_L = j\omega L i_L$$

Comparing the equation (similar to that of  $V = IR$ )

$$j\omega L = jX_L = Z_L$$

$X_L$  is called as reluctance (in ohm) of an inductor

- When  $\omega = 0$ ,  $X_L = 0$ , means reactance is zero and inductor behaves like a **short at DC**
- When  $\omega = \infty$ ,  $X_L = \infty$ , means inductor behaves like an **open circuit** at higher frequencies
- Frequency dependent electrical behavior of inductance on circuit



$$p_L = v_L i_L = L i_L \int_{t_0}^{t_1} i_L dt$$

$$w_L = \int_{-\infty}^t p_L dt = \int_{-\infty}^t L \frac{di_L}{dt} i_L dt = L \int_{-\infty}^t i_L di_L = \frac{1}{2} L i_L^2$$

# Inductors in Series

- Consider inductors connected in a series configuration as shown in the circuit

- Applying KVL

$$v = v_1 + v_2 + v_3$$

- Noting the relation between voltage across and current through inductor,


$$v_1 = L_1 \frac{di}{dt} \quad v_2 = L_2 \frac{di}{dt} \quad v_3 = L_3 \frac{di}{dt}$$

- If  $L_{eq}$  is the total inductance of the circuit, then

$$v_{in} = L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3$$

$$L_{eq} = \sum_{s=1}^N L_s$$

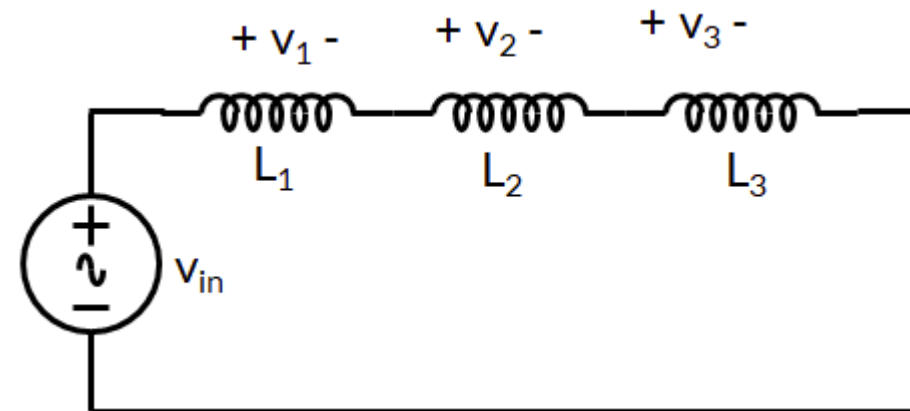

# Inductors in Parallel

- Consider inductors connected in a parallel configuration as shown in the circuit

- Applying KCL

$$i_{in} = i_1 + i_2 + i_3$$


- Noting the relation between voltage across the inductor and current through inductor

$$i_1 = \frac{1}{L_1} \int_{t_0}^{t_1} v dt \quad i_2 = \frac{1}{L_2} \int_{t_0}^{t_1} v dt \quad i_3 = \frac{1}{L_3} \int_{t_0}^{t_1} v dt$$

- If  $L_{eq}$  is the total inductance of the circuit, then

$$i_{in} = \frac{1}{L_{eq}} \int_{t_0}^{t_1} v dt = \frac{1}{L_1} \int_{t_0}^{t_1} v dt + \frac{1}{L_2} \int_{t_0}^{t_1} v dt + \frac{1}{L_3} \int_{t_0}^{t_1} v dt \quad \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$
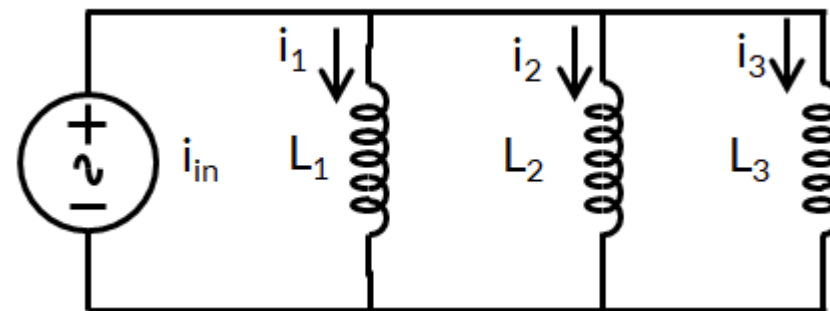
$$L_{eq} = \left( \sum_{p=1}^N \frac{1}{L_p} \right)^{-1}$$



# Charging of an Inductor

- Consider the circuit shown in figure
- Applying KVL

$$V_0 = V_R + V_L$$

$$V_0 = iR + L \frac{di}{dt}$$

$$\frac{Ldi}{V_0 - Ri} = dt$$


$$\int \frac{Ldi}{V_0 - Ri} = \int dt$$

$$-\frac{L}{R} \ln(V_0 - Ri) = t + k$$

Using the initial boundary condition: at time  $t = 0$ ,  $i(t)=0$

$$k = -\frac{L}{R} \ln V_0$$
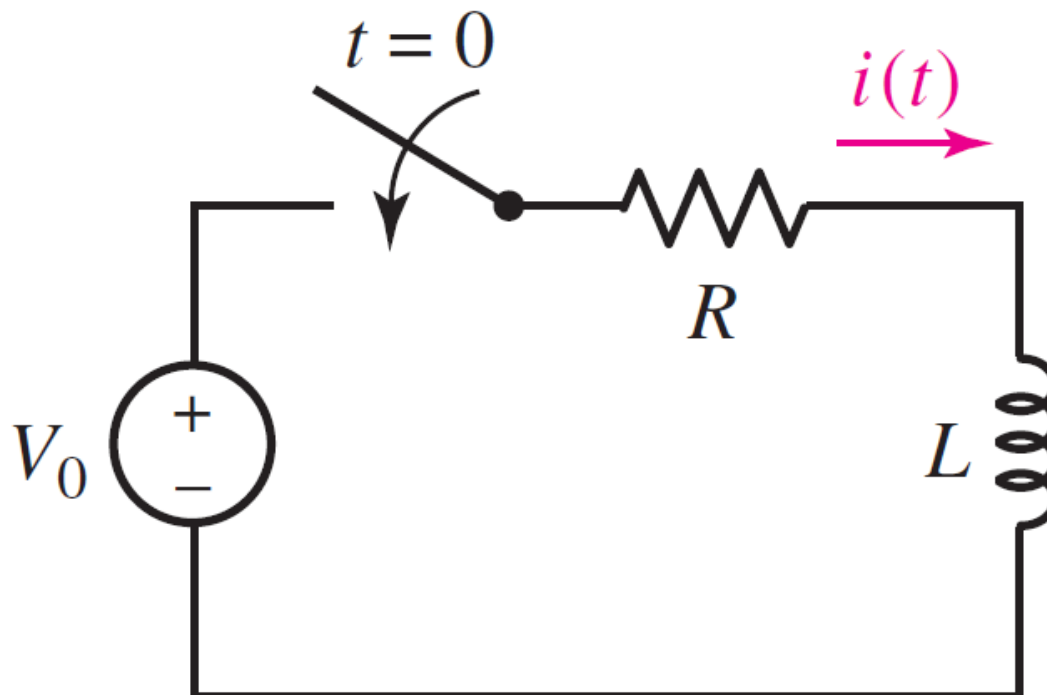
$$-\frac{L}{R} \ln[(V_0 - Ri) - \ln(V_0)] = t \Rightarrow \frac{V_0 - Ri}{V_0} = e^{-\frac{Rt}{L}} \Rightarrow i = \frac{V_0}{R} (1 - e^{-\frac{Rt}{L}})$$



## Discharge Current through an Inductor

Applying KVL to the circuit:

$$v(t) + Ri(t) = 0$$

$$L \frac{di(t)}{dt} + Ri(t) = 0$$


$$\frac{di(t)}{i(t)} = -\frac{R}{L} dt$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} t$$

$$i(t) = I_0 e^{-\frac{R}{L} t}$$

Time constant  $\tau$  is given by

$$\tau = \frac{L}{R}$$

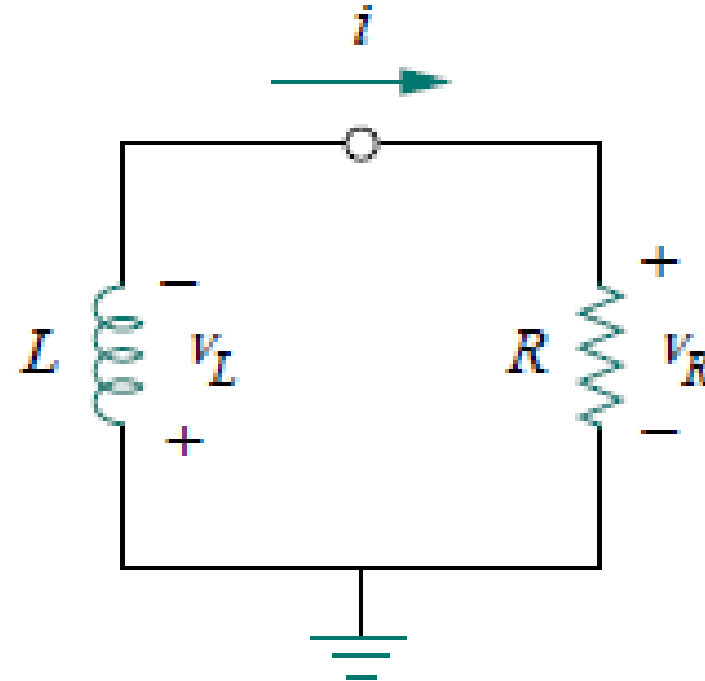

## Discharge Current through an Inductor

