

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-12

Topics Covered: Introduction to semiconductor devices and Diode circuits

Material Constants of Si: $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, $\mu_n = 1500 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$, $\mu_p = 500 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$. $E_G = 1.12 \text{ eV}$.

Universal Constants: Unit charge (q) = $1.6 \times 10^{-19} \text{ C}$, Boltzmann constant (k) = $1.38 \times 10^{-23} \text{ JK}^{-1}$.

If not mentioned, assume non-ideality factor (η) as 1.5, reverse saturation current I_0 as 5 nA.

1. In a piece of silicon semiconductor, Fermi level lies 0.7 eV away from the conduction band. Answer the following questions.
 - i) Find electron density and hole density.
 - ii) Find conductivity and resistivity.
2. A p-type silicon bar having a resistivity of $0.25 \Omega\cdot\text{cm}$ and an n-type silicon bar having a resistivity of $0.1 \Omega\cdot\text{cm}$ are used to form a PN Junction. Answer the following questions.
 - i) Find majority carrier concentration and minority carrier concentration on each side of the junction.
 - ii) What is the built-in potential of the diode?
3. The reverse saturation current for a set of diodes varies between $5 \times 10^{-14} \leq I_0 \leq 5 \times 10^{-12}$ A. The diodes are all to be biased at 2 mA. What is the range of forward voltages that must be applied?
4. A PN junction diode having reverse saturation current of 10^{-11} A is forward biased so that the current through the diode is $150 \mu\text{A}$. Find the diode voltage.
5. At what reverse bias voltage does the reverse bias current in a PN Junction reaches 90% of its reverse saturation current?
6. What is the ratio of the current for a forward-bias voltage of 0.2 V to the current for a reverse-bias voltage of 0.2 V?

7. For the diode circuit shown in Fig. 1, $V_S = 2$ V. The silicon diode has a reverse saturation current of 1 nA at 300 K. Given that $V = 0.7$ V. Find

i) R_2 when $R_1 = 1$ k Ω and ii) R_1 when $R_2 = 1$ k Ω

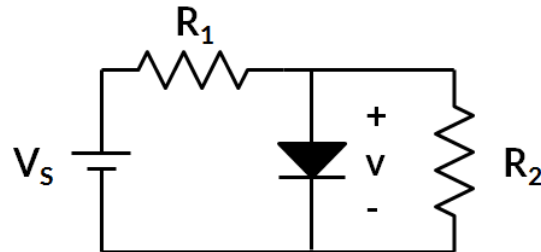


Fig. 1.

8. The diode circuit shown in Fig. 2, D_1 and D_2 are silicon diodes having saturation currents of 5 nA and 10 nA, respectively, at 300 K. Given that both the diodes are forward biased. Find the values of R for which the current is 15 mA.

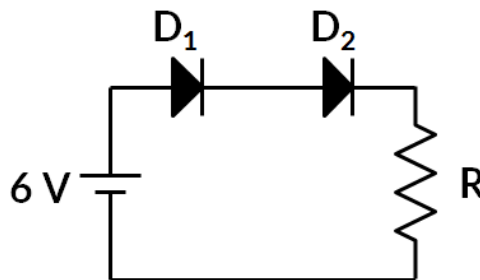


Fig. 2.

9. For the ideal diode circuit shown in Fig. 3, let $R_f = 1$ k Ω and $R = 9$ k Ω . Find the output voltage V_0 when

- i) $V_1 = V_2 = 0$ V
- ii) $V_1 = 10$ V, $V_2 = 0$ V
- iii) $V_1 = V_2 = 10$ V

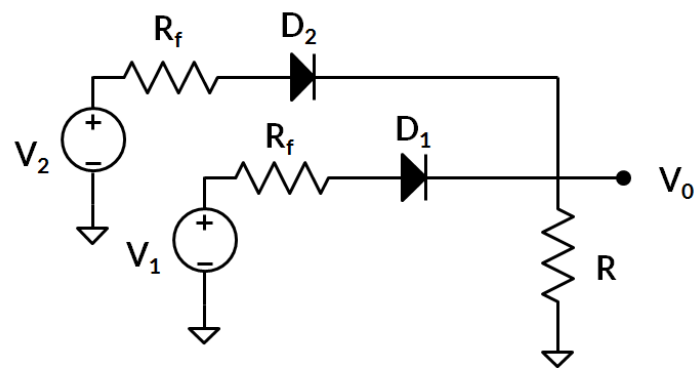


Fig. 3

10. Consider the circuit shown in fig. 4. Determine the current through the diode and voltage across the diode. Assume that the cut-in voltage of the diode is 0.6 V.

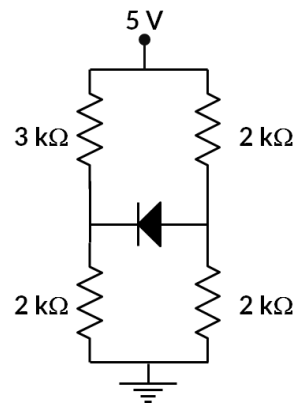


Fig. 4

11. The reverse saturation current of each diode in fig. 5 is 2×10^{-10} A. Determine the input voltage required to produce an output voltage of 0.60 V.

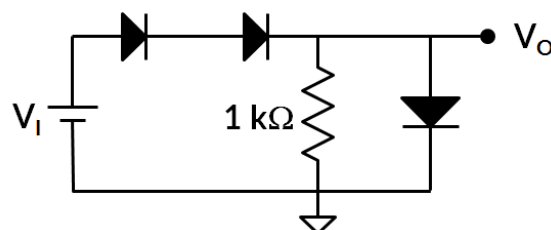


Fig. 5

12. Assume that each diode in the circuit shown in fig. 6 has a cut-in voltage of 0.65 V.
- If the input voltage is $V_i = 5$ V, determine the value of R_1 such that I_{D1} is one-half of I_{D2} . What are the values of I_{D1} and I_{D2} ?

ii) If $V_1 = 8\text{V}$ and $R_1 = 2\text{ k}\Omega$, determine I_{D1} and I_{D2} .

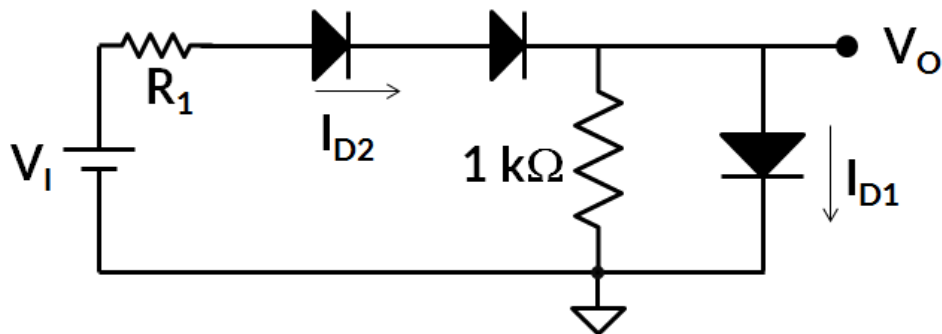


Fig. 6

13. In the circuit shown in fig. 7, find the diode voltage V_D and the supply voltage V such that the current $I_D = 0.4\text{ mA}$. Assume cut-in voltage is 0.7V . What is the power dissipated by the diode?

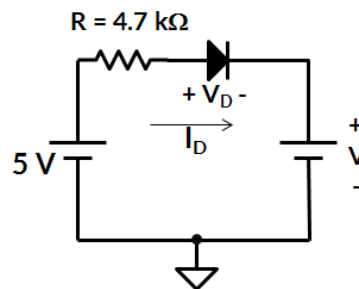


Fig. 7

----- END OF QUESTIONS -----

Answers:

- 1) (i) Electron density = $6.9 \times 10^7\text{ cm}^3$, Hole density = 1.5×10^{10}
(ii) Resistivity = $2.61\text{ }(\Omega\text{-cm})^{-1}$, conductivity = $3.82\text{ k}\Omega\text{-cm}$
- 2) (i) $N = 4500\text{ cm}^{-3}$, $p = 5400\text{ cm}^{-3}$, (ii) 0.78 V
- 3) $0.515\text{ V} - 0.634\text{ V}$
- 4) 0.43 V
- 5) -0.06 V
- 6) 2193.4
- 7) i) $R_2 = 538\text{ }\Omega$, ii) $R_1 = 1.86\text{ k}\Omega$
- 8) $R = 350\text{ }\Omega$
- 9) i) $V_O = 0\text{ V}$ ii) $V_O = 8.46\text{ V}$ iii) $V_O = 8.91\text{ V}$

10) $I_D = 0 \text{ A}$, $V_D = 0.5 \text{ V}$

11) $V_I = 1.378 \text{ V}$

12) i) $I_{D1} = 0.65 \text{ mA}$, $I_{D2} = 1.3 \text{ mA}$, $R_1 = 2.35 \text{ k}\Omega$ ii) $I_{D1} = 2.375 \text{ mA}$, $I_{D2} = 3.025 \text{ mA}$

13) $V = 2.42 \text{ V}$, $P = 0.28 \text{ mW}$