

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-3

1. For the circuits shown in fig. 1 through 4, find the equivalent resistance  $R_T$  between nodes A and B. If the value for any resistor is not provided, assume  $1\text{ k}\Omega$  resistance.

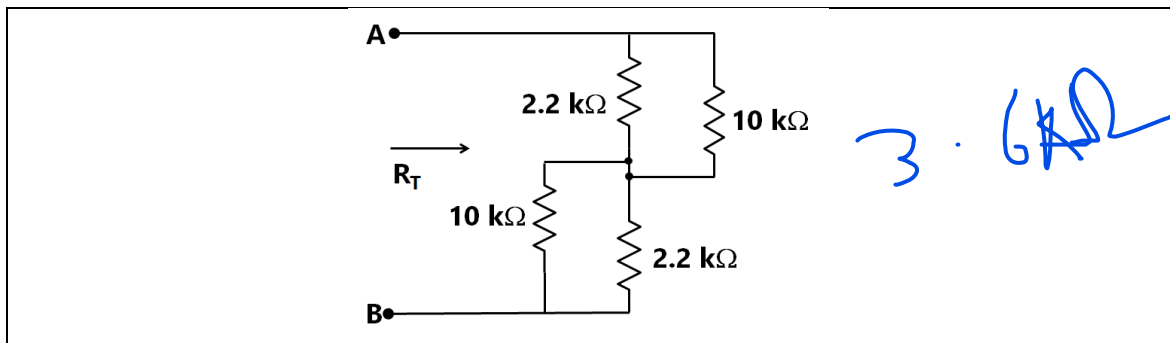


Fig. 1

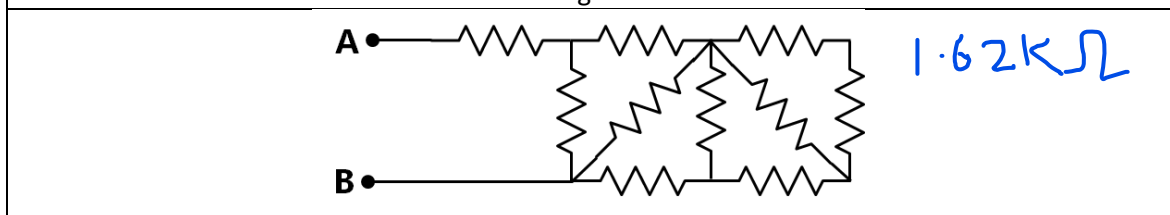


Fig. 2

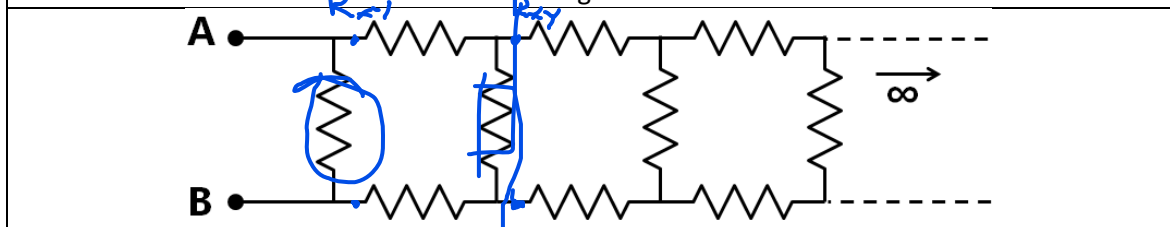


Fig. 3

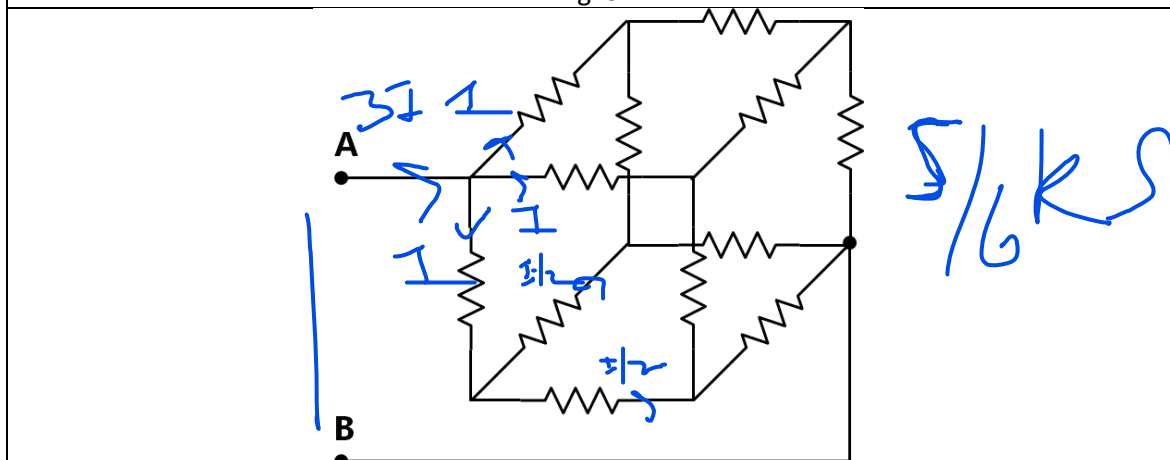


Fig. 4

2. For the circuit shown in fig. 5 through 8, find the equivalent resistance between nodes A and B. Then evaluate current through each resistor and voltage drop across each resistor.

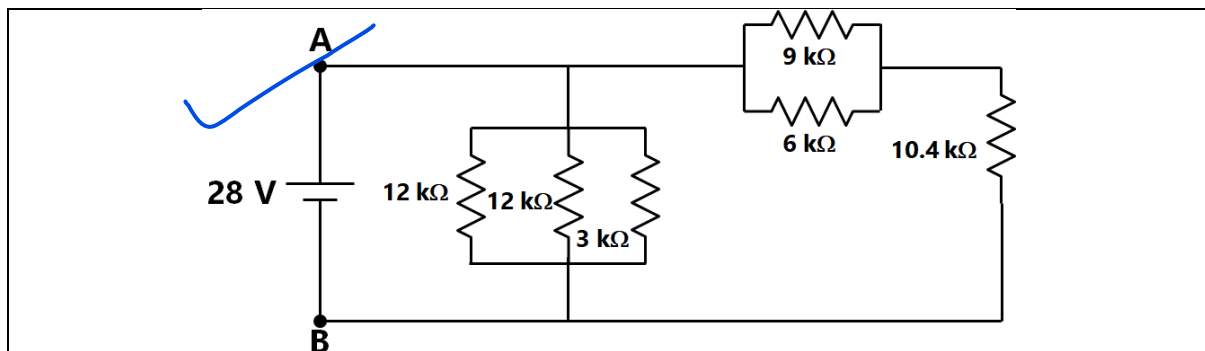


Fig. 5

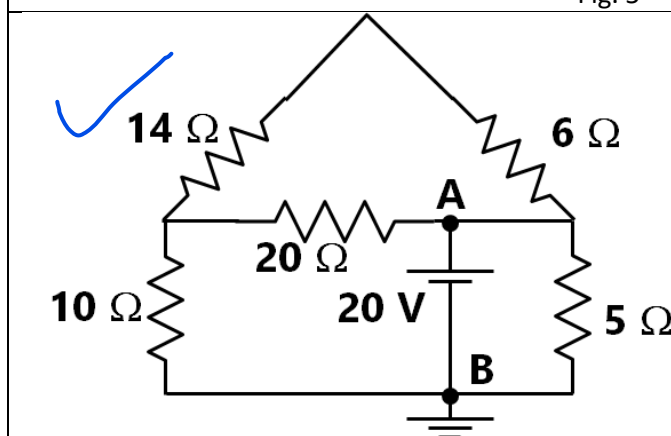


Fig. 6

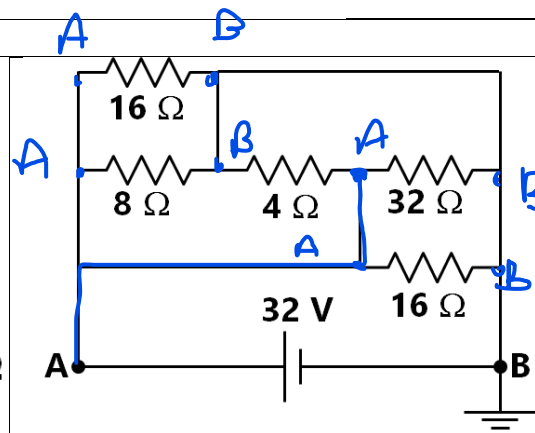


Fig. 7

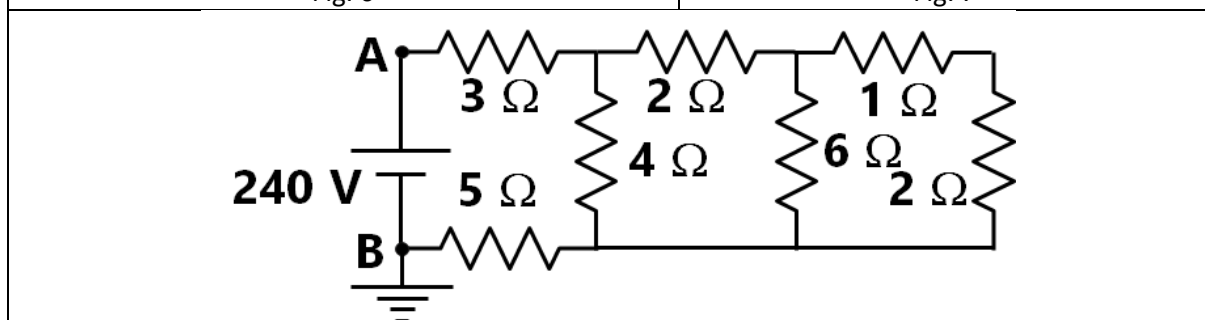


Fig. 8

3. For the circuit shown in fig. 9 and fig. 10, determine current through the resistors, voltage across the resistors and their power rating.

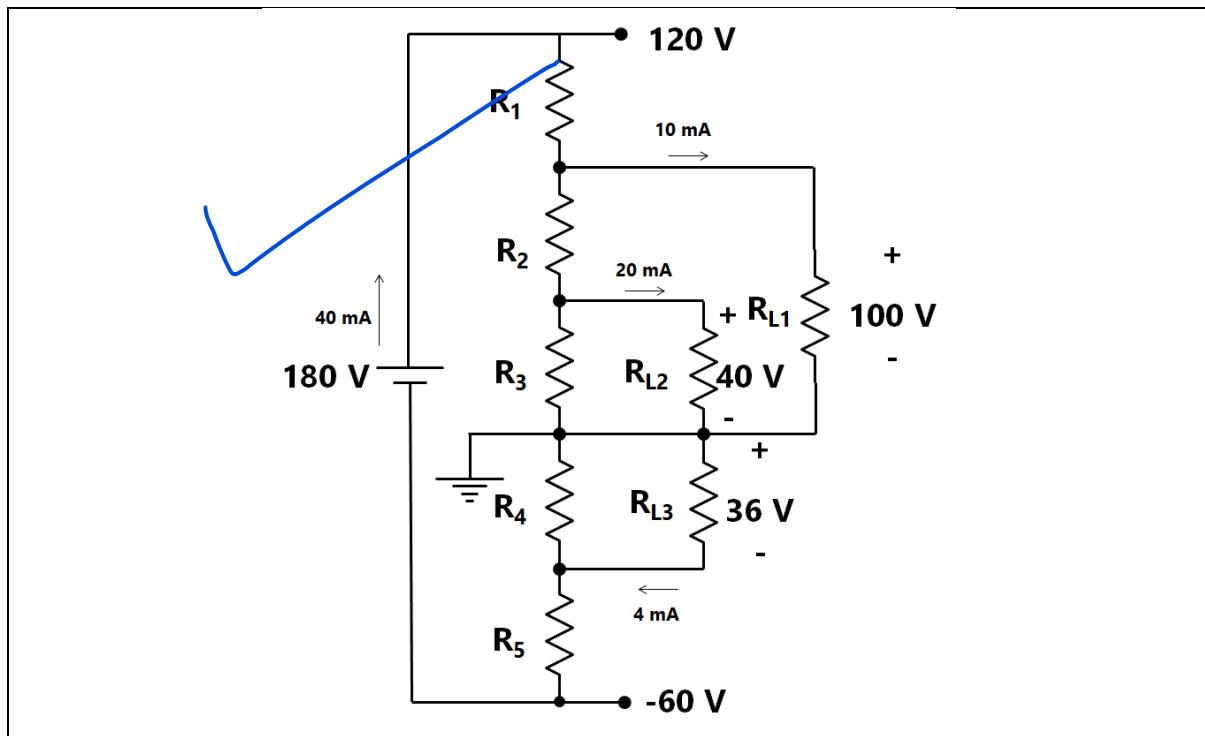


Fig. 9

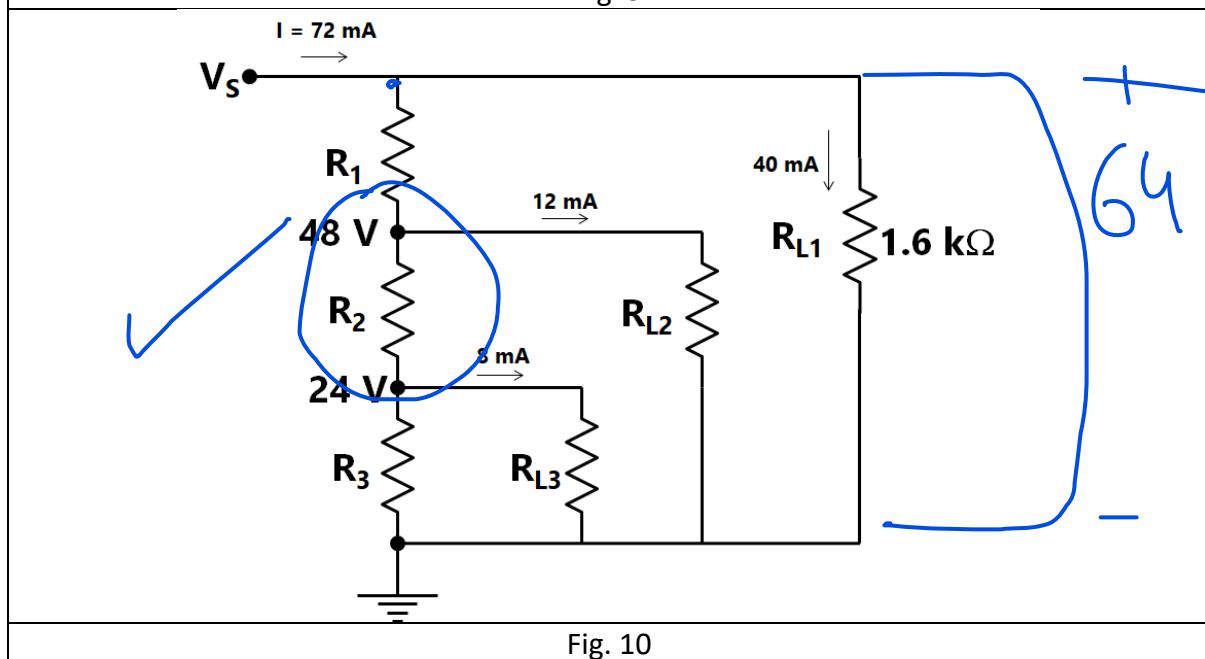


Fig. 10

----- END OF QUESTIONS -----

### Answers:

Question 1:

Figure 1:  $R_T = 3.6 \text{ k}\Omega$

Figure 2:  $R_{AB} = 1.62 \text{ K}\Omega$

Figure 3:  $R_{AB} = 0.732 \text{ R}\Omega$

Figure 4:  $R_{AB} = (5/6)R \text{ k}\Omega$

Question 2:

Figure 5:  $R_{AB} = 1.75 \text{ K}\Omega$

Resistor	Current through the resistor	Voltage across the resistor
10.4 K $\Omega$	2 mA	20.8 V
9 K $\Omega$	0.8 mA	7.2 V
6 K $\Omega$	1.2 mA	7.2 V
12 K $\Omega$	2.33 mA	27.96 V
3 K $\Omega$	9.34 mA	28.02 V

Figure 6:  $R_{AB} = 4 \text{ }\Omega$

Resistor	Current through the resistor	Voltage across the resistor
14 K $\Omega$	0.5 A	7 V
10 K $\Omega$	1 A	10 V
6 K $\Omega$	0.5 A	3 V
20 K $\Omega$	0.5 A	10 V
5 K $\Omega$	4 A	20 V

Figure 7:  $R_{AB} = 16/3 \text{ }\Omega$

Resistor	Current through the resistor	Voltage across the resistor
16 $\Omega$ (R1)	2 A	32 V
8 $\Omega$	4 A	32 V
4 $\Omega$	0	0
32 $\Omega$	0	0
16 $\Omega$ (R5)	0	0

Figure 8:  $R_{AB} = 10 \Omega$

Resistor	Current through the resistor	Voltage across the resistor
1 $\Omega$	8 A	8 V
2 $\Omega$ (R4)	12 A	24 V
2 $\Omega$ (R7)	8 A	16 V
3 $\Omega$	24 A	72 V
4 $\Omega$	12 A	48 V
5 $\Omega$	24 A	120 V
6 $\Omega$	4 A	24 V

Question 3:

Figure 9

Resistor	Current through the resistor	Voltage across the resistor	Power rating
R <sub>1</sub>	40 mA	20 V	0.8 W
R <sub>2</sub>	30 mA	60 V	1.8 W
R <sub>3</sub>	10 mA	40 V	0.4 W
R <sub>4</sub>	36 mA	36 V	1.296 W
R <sub>5</sub>	<del>36 mA</del> 40 mA	24 V	0.96 W

Figure 10

Resistor	Current through the resistor	Voltage across the resistor	Power rating
R <sub>1</sub>	32 mA	16 V	0.512 W
R <sub>2</sub>	20 mA	<del>48 V</del> 24 V	0.96 W
R <sub>3</sub>	12 mA	24 V	0.288 W
R <sub>L1</sub>	40 mA	64 V	2.56 W
R <sub>L2</sub>	12 mA	48 V	0.576 W
R <sub>L3</sub>	8 mA	24 V	0.192 W